Circuit Playground Lesson #0 Created by lady ada



Last updated on 2016-08-30 07:36:12 PM UTC

Guide Contents


Guide Contents	2
Intro	5
Hi there!	5
Who is this for?	6
What is a Circuit Playground?	6
Who are you?	7
About This Lesson	8
Lesson Parts	9
Required:	9
Not Required but Recommended!	10
Take a Tour!	12
The Parts of a Circuit Playground	12
Microcontroller	14
Main Chip / Microcontroller	14
Our Pal, the ATMEGA32u4	16
Simplicity & Sturdiness	17
Battery Jack & Supply	19
Battery Power Jack	19
Onboard Power Supply	21
Output Current	23
USB Connection	25
USB Jack	25
USB Inteface Chip??	26
Powering over USB	27
Basic LEDs	29
Circuit Playground Basic LEDs	29
Library Reference	30
Reset Button & Bootloader	31
Re-starting/Resetting	31
Bootloader Mode	31
Buttons & Slide Switch	33

© Adafruit Industries https://learn.adafruit.com/circuit-playground-lesson-number-0

Two Pushbuttons	33
Slide Switch	34
Library Reference	34
slideSwitch	34
leftButton and rightButton	34
NeoPixels	36
Library Reference	37
setPixelColor	37
clearPixels	37
setBrightness	37
Temperature Sensor	39
Library Reference	40
Light Sensor	41
Library Reference	42
Sound Sensor	43
Library Reference	44
Mini Speaker	45
Library Reference	46
Accelerometer	47
Library Reference	48
Motion in X Y and Z	48
Setting Accelerometer Range	48
Tap Detection	48
Alligator Pads & Pinout	49
Capacitive Touch	50
Library Reference	50
Pad Usage (pinout)	50
Left Side	50
Right Side	51
Power Up Test	53
Bootloader Reset Test	55
Download Software	57
Windows	57
Mac	57

Linux	58
Raspberry Pi and other ARM-based Linux	58
Install Software (Windows)	59
Installing Arduino	59
Circuit Playground Driver	62
Find your Serial (COM) Port	64
Install Software (Mac OS X)	67
Installing Arduino	67
No Drivers To Install!	68
Find your Serial Port Device	68
Install Software (Linux)	70
Installing Arduino	70
Driver Installation	72
Verify your Serial Port	73
udev Rules	74
Add Circuit Playground to Arduino	76
Open up Preferences Menu	76
Add the Adafruit Board Support package!	77
Manage Board Support	78
Add Circuit Playground Library	80
Library Reference	83

Intro

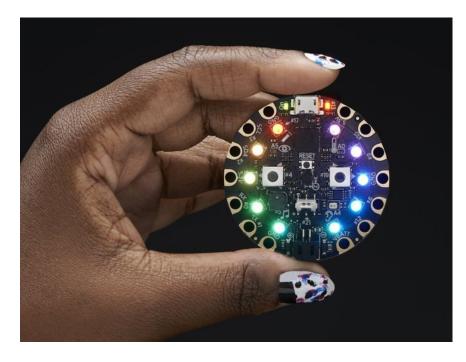

Hi there!

If you're here, it's because you want to learn how to build and make stuff with electronics! (If, rather than learn electronics, you'd like to look at pictures of cats instead, please check https://www.adafruit.com/galleries/cats-of-engineering (http://adafru.it/oAd))

And, you're in luck: there's never been a better time.

Gone are the days where you need thousands of dollars of equipment and lots physics/math background. Nowadays, if you want to learn to work with electronics, you can jump right in for \$20 or less, and any sort of computer. And we're talking about learning *a lot* of electronics - from the basics of analog to the complexities of firmware. With a good

pack of parts, you can build a base of knowledge that will take you from your first blinking LED to someone who can start prototyping and inventing custom products.

Who is this for?

Anyone with a computer they can install software on, an Arduino or compatible and the ability to type and click a mouse. That's pretty much the minimum.

You don't need to know a lot of physics or math and just like an Art Degree isn't required for making art and being creative, you don't need to have a computer science degree. It helps if you're comfortable using computers but that's a skill most people pick up through life.

If you know how to program already - great! If not, don't worry, we'll teach you enough to be dangerous.

What is a Circuit Playground?

Circuit Playground is the name of the little round electronic circuit board that you are going to use as a tool to investigate and explore programming & electronics. Think of it as like a Swiss Army Knife or multi-tool for learning electronics as an art form! It is an all-in-one board so you can jump in quickly and do a whole lotta projects (It can slice, it can dice, it has lots of blinky LEDs!)

Circuit Playground can light up multicolored LEDs (make beautiful lighting effects), make sounds (like a synthesizer!), detect touch or color, sense the environment like temperature, sound, and motion, and more!

By programming your Playground with software, you can combine all these abilities. For example, it can use the sound sensor to listen to music, and then pulse the LEDs to react to the melody and rhythm it hears. Or, you can use the motion sensor to detect when someone moves your purse and play a loud alarm to scare them off!

Circuit Playground works with the Arduino software. You can use the Arduino IDE software to program Circuit Playground. The main chip in Circuit Playground is natively supported, which means you can use the thousands of projets and tutorials seamlessly!

Best of all, no soldering required! You do not need *anything* to get started other than a Circuit Playground, a common USB cable and any computer (Windows/Mac/Linux/Chromebook)

Who are you?

Great question. This is me:

I'm Ladyada, and I love to teach people how to build stuff and how they can be creative with technology.

So, are you ready?

Let's do this thing!

About This Lesson



MODERN HOME No. 115


This lesson won't teach any electronics, really. Its more for making sure that everything is setup and *ready* for the future lessons. It will verify the Circuit Playground is working as intended and that the computer you are using is compatible.

Think of this tutorial as the **'home base'** of your journey. If things ever get into a weird spot come back here and re-verify this lesson!

One of the most important skills you'll have to learn is that when things go wrong (and they will, *tons*) come back to the most basic assumptions. This is a little bit of the "are you sure its on" of electronics. It's surprising how many skilled engineers will spend hours debugging a circuit to realize that...it wasn't plugged in!

Lesson Parts

Required:

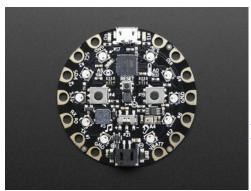

A **Circuit Playground!** Of course, this is essential, and is required for all lessons.

Available at
Adafruit (http://adafru.it/3000)



Micro USB Cable any length. You probably have one of these around, they're the most common USB cable.

Make sure its a data/sync cable!

USB cable available at Adafruit (http://adafru.it/592)

A HUUUUUUGE number of people have problems because they pick a 'charge only' USB cable rather than a "Data/Sync" cable. Make 100% sure you have a good quality syncing cable. Srsly, I can't even express how many times students have nearly given up due to a flakey USB cable!

Not Required but... Recommended!



If you'd like to power your Playground for portable use, you can use a 3 x AAA battery holder with a JST PH-2 connector on it. These holders even come with an on/off switch so you can save battery when not in use.



Of course, 3 AAA batteries are required as well. Circuit playground works best with Alkaline or rechargeable NiMH




batteries.

You can also use other AAA batteries such as Zinc or Lithium. NiCad batteries are not recommended.

Please use rechargeable batteries if you can, to reduce waste!

Take a Tour!

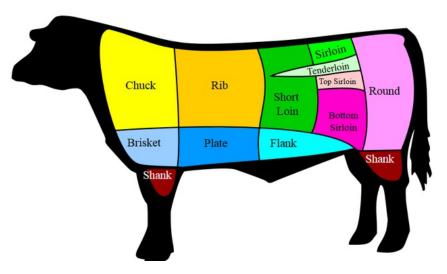


It's handy to know the names for parts of a cow when talking about cuts of meat!

Here we'll take a tour and point out the names of the Circuit Playground. You'll want to refer back to this page a ton, so keep it handy when we say something like "JST connector" or "Reset button"

The Parts of a Circuit Playground

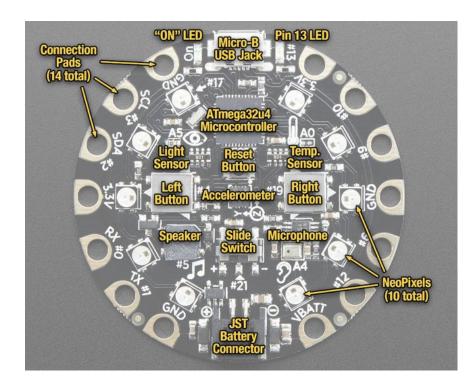Here's a rough version of the parts of an Circuit Playground we'll refer to. Each part is covered in more detail in the next sections




Microcontroller

Don't feel like you have to understand this part fully! Skim it for now, and consider it a resource for you when you want to take a deeper dive into understanding the hardware!

Main Chip / Microcontroller

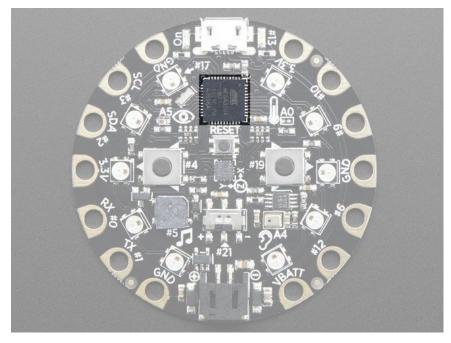
This is the 'brains' of the Circuit Playground. The thing that you program when you program! It's what runs the code, the **CPU** (Central Processing Unit). Kinda like the processor that runs in your computer but much much much simpler and smaller.



The chip has very thin little *legs* that go around it, you can see the little silver dots that connect each leg of the microcontroller to the circuit board. Those dots both mechanically *and* electrically connect the CPU - so it can send data to and from your computer and those

sensors and lights.

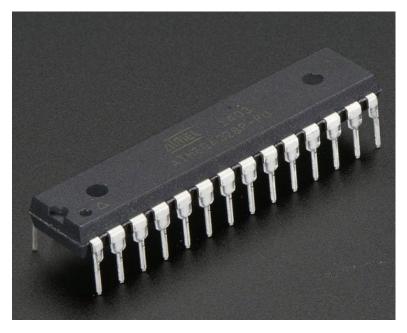Each one of those mini legs are called pins because older microcontrollers used to look like this:



Where each of the legs really do look like sharp pins. Those older microcontrollers are really big, though. And so over time the 'controllers got hit with a shrink ray until they looked like this:

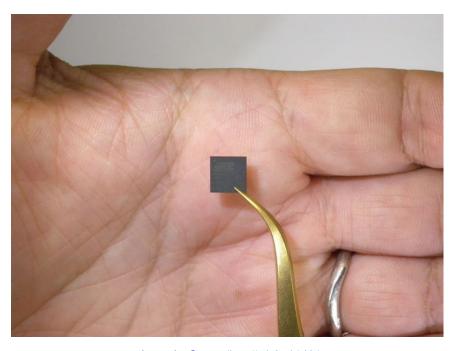


Image by Osamu (http://adafru.it/oVe)

Yep that little square has all the circuitry of the bigger chip, but so small you have to use tweezers to pick it up!

Our Pal, the ATMEGA32u4

The Circuit Playground microcontroller is called the ATmega32u4 and it has:

- 44 Pins
- Powered by 3 Volts
- Requires about 0.1 Watts of power
- Runs at 8 MHz
- 32 KB of flash storage
- ~2 KB of RAM
- Costs about \$5 per

Compare this to, at the time of writing, a commoncomputer chip, the Intel i5-6400



- 1151 Pins
- Powered by 1.35 Volts
- · Requires about 35 Watts of power
- Runs at 2800 MHz
- No internal Flash storage, but most computers have at least 250 GB = 250,000 MB = 250,000,000 KB* of storage
- No internal RAM but most computers have at least 4 GB = 4,000 MB = 4,000,000* KB of RAM
- Costs about \$200

(* yes I know its not exactly 1000)

So, clearly if you want an ultra powerful computer processor that can play the latest games, an i5 is the way to go. But its expensive, and requires a ton of power, and you need to have a full motherboard to run it so it's kinda big. If you just want to do some simple tasks, a microcontroller like the '32u4 is peachy. Also, its quite handy that it has the RAM and storage inside of it - its not a lot but that means you don't need to hook up a hard drive to this chip, its very compact and complete.

Simplicity & Sturdiness

What's cool about the microcontroller is that unlike your computer which requires an operating system (Mac OS X or Windows) and booting up, the microcontroller is 'barebones'. When you plug it in, it immediately runs whatever code you asked it to do.

And, you don't have to worry about a diskette or hard drive or cd-rom getting scratched or damaged. The storage inside of the chip lasts for a really long time. You could program your Arduino, leave it alone for decades, even hundreds of years & come back and power it up with a post-apocalyptic-cyber-battery and it would work just as new.


Battery Jack & Supply

Don't feel like you have to understand this part fully! Skim it for now, and consider it a resource for you when you want to take a deeper dive into understanding the hardware!

Battery Power Jack

There are two ways to power your Circuit Playground: you can use the USB connector to connect to a computer or portable USB power pack *or* you can plug in a battery pack. USB can be used to power and program. The battery connection can only be used for power -but it's great for when you want to take your Circuit Playground out into the world

This is the Battery Power Jack:

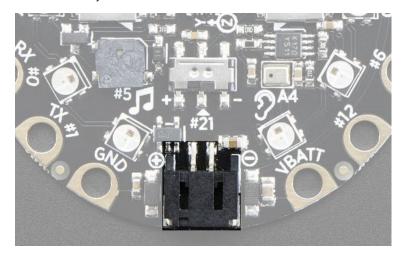


The technical specifications for the jack is:

JST PH type 2-pin connector Pin #1 Power and Pin #2 Ground

You can use this with any battery pack that can provide at least 3.5V DC and up to 6.5V DC. In particular it works really well with 3 \times 1.5V batteries, like this 3 \times AAA battery holder



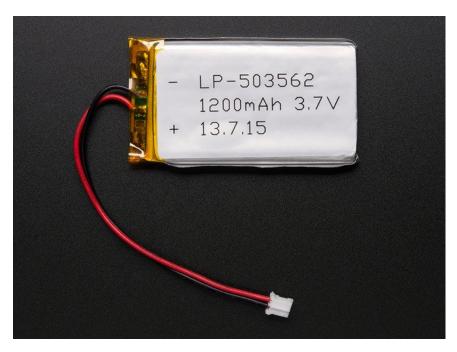Advanced users can connect up a single-cell rechargeable lithium ion or lithium polymer battery




Lithium Ion or Polymer batteries are more difficult to use and require much more care than rechargeable AAA's so we don't recommend them.

Circuit Playground does not have battery charging built inso no matter what rechargeable battery you have, you will need a separate charger as well.


Onboard Power Supply

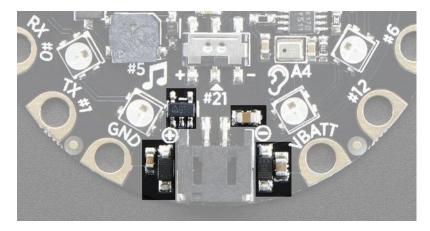Circuit Playground is designed for beginners so it has some protection and *regulation* circuitry so that it is flexible about how it is powered. In particular there is a polarity protection diode (to avoid destroying the board if you have a backwards-connected battery). It also has an **onboard 3.3V Power Supply:**



This means you can power it from anywhere between 3.5V up to 6.5V and it will automatically *regulate* it down to a clean 3.3V

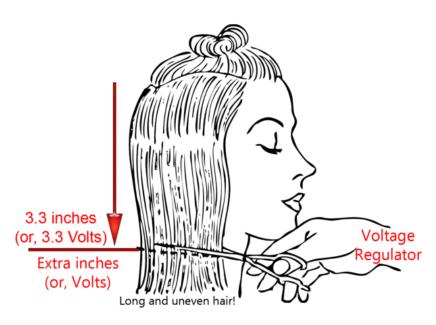Think of it like a barber. When you go to the hair salon, you have long uneven hair (just like the large, uneven power that is fed into the Circuit Playground from a battery pack). The stylist takes out the scissors and says **OK how long do you want your hair?** and you reply **3.3 inches long!**



>snip snip< and your hair is cut straight off, leaving a very clean line.

Just make sure all of your hair, err... battery voltage is at least 3.5 Volts because the regulator needs some extra length to work with.

The Circuit Playground will work off of battery or USB, and can have both plugged in at once - it will automatically switch to whichever is the higher voltage

Output Current

When powering Circuit Playground, you can draw at most 500 milliAmps of current. This is not a guarantee because you also have to make sure that the regulator doesn't overheat. If you're using some other voltage input, the max current you can pull continously is approximately

250 milliWatt / (Input Voltage - 0.3 - 3.3 V) = in milliAmps

So for 5V USB in, the max for *continuous* current is 250/(5-0.3-3.3) = 178 milliAmps


This is just a rough estimate and depends on if the power usage is continuous or just once

in a while.

USB Connection

Don't feel like you have to understand this part fully! Skim it for now, and consider it a resource for you when you want to take a deeper dive into understanding the hardware!

The USB Jack is next up in our tour

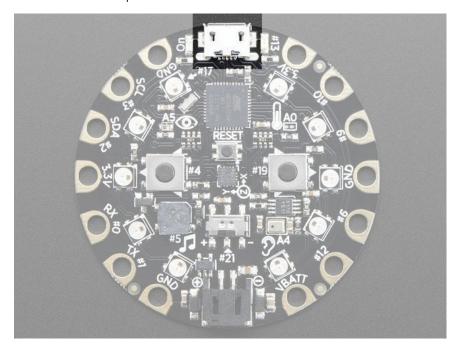

USB Jack

As we talked about in the beginning, this is how you connect your Arduino to your computer. You can use any computer with a USB port. You will need a cable to connect! This cable is usually not included.



Make sure you have a Micro USB cable

A HUUUUUUGE number of people have problems because they pick a 'charge only' USB cable rather than a "Data/Sync" cable. Make 100% sure you have a good quality syncing cable. Srsly, I can't even express how many times students have nearly given up due to a flakey USB cable!

I can't stress it enough. Make sure you have a good USB cable. Naughty USB cables will really ruin your day, like a stone in your shoe. Just thow out bad cables and replace with a good one - they are designed to be disposable!

USB Inteface Chip??

If you're coming from any background with an Arduino you're used to having a secondary chip on the circuit board that acts as the **USB to Serial Interface Translator chip**. Circuit Playground does not have one of these! That's because the ATmega32u4 processor does the USB for you *natively* without the need for a second chip. There's a few tradeoffs, in

particular you may need to reset the chip if the USB crashes but you'll learn how to do that

Powering over USB

For permanent installation, you can power your Circuit Playground using a USB wall adapter - these come with almost every phone and gadget these days. They have a nice clean 5V output. Some have an output up to 5.5V but thats OK. Basically, if it has a USB connection it will power your 'play just fine!



You can *sometimes* power an Circuit Playground project off of a portable USB power pack but these packs are often designed to charge a phone and the 'Play uses so little power that it will cause the pack to think that it is "done charging" and auto-shutoff



So, try it out but your mileage may vary.

Basic LEDs

Don't feel like you have to understand this part fully! Skim it for now, and consider it a resource for you when you want to take a deeper dive into understanding the hardware!

Your Circuit Playground has some lights that it can use to give you an idea of what it is up to.

These lights, called **LEDs** (pronounced Ell Eee Dee), are on just about every electronic device you own. Often times they're used to let you know if something is on and if there's an error. For example, here's a cable modem with multiple LEDs.


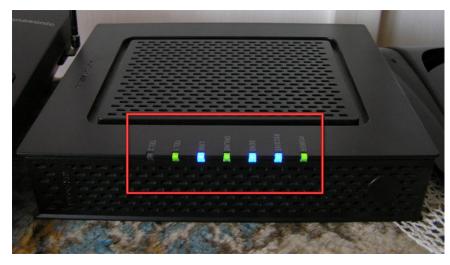


Image from Wikipedia (http://adafru.it/oBB)

Each LED indicates the status of the modem. For example, on this device the one to the right is the **POWER** LED, its lit if there's good power. In the middle is the**ONLINE** LED, which lets you know if the modem was able to connect to the Internet.

Circuit Playground Basic LEDs

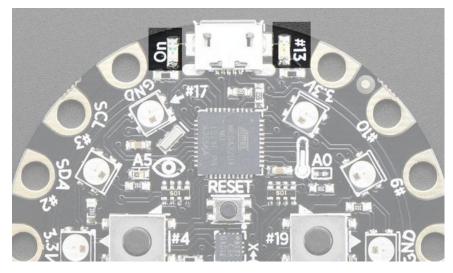Likewise, the Circuit Playground has two basic (single-color) LEDs: ON and #13



They sit to the left and right of the Micro USB jack

ON LED - this LED will shine green whenever the Circuit Playground is powered. Always check this LED if your board is not acting right, if its flickering or off then you should check your power supply

#13 LED - this is the one LED that you can control. The ON lights up automatically no matter what. The **#13** LED, however, is connected to one of the main microcontroller's pins and you can turn it on or off when you start writing code. This LED also pulses to let you know when the *bootloader* is active and ready to receive a program

It's called lucky #13 because it is connected to pin number 13 on the microcontroller!

Library Reference

You can turn the #13 LED on by calling the procedureCircuitPlayground.redLED(true) and turn it off with CircuitPlayground.redLED(false)

© Adafruit Industries

https://learn.adafruit.com/circuit-playground-lesson-number-0

Page 29 of 83

© Adafruit Industries

https://learn.adafruit.com/circuit-playground-lesson-number-0

Page 30 of 83

Reset Button & Bootloader

There's a special mini button labeled **RESET** right below the microcontroller. This is the, well, *reset* button. It will perform a clean restart of the microcontroller or let you start the bootloader by hand.


Re-starting/Resetting

To re-start your Circuit Playground (basically, same as turning it off and back on again) - **click the reset button once**. The Circuit Playground will restart itself.


Bootloader Mode

To start the Circuit Playground bootloader -click the reset button twice. The bootloader will run for 10 seconds during which time you can upload new code. You shouldn't have to do this unless something got a little confused in the 'Play, but its an essential skill! During bootloader mode, the red #13 LED will breate on and off once a second.

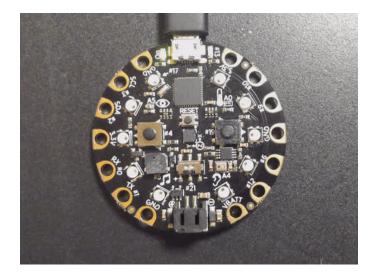It's good to practice both resetting (single click) and bootloading (double click). Check the Power Up test page for more details. (http://adafru.it/pdH)



Buttons & Slide Switch

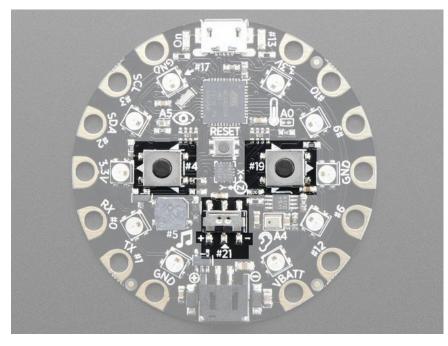

Now we're starting to get to the sensors built into the Circuit Playground. These are parts that are normally *not* included on an Arduino-like board. They are yours to play with and use as you travel on the path of learning!

Two Pushbuttons




There are two momentary pushbuttons, you can use these in any of your projects to change modes, indicate when to start or stop a sketch, modify behavior, really anything!

- The Left button is connected to digital pin#4
- The Right button is connected to digital pin#19

Both have $10K\Omega$ *pull-down* resistors. That means that when the button is *pressed* the value read off those pins will be 'high'. You'll learn more about that later, but its here for your reference

Slide Switch

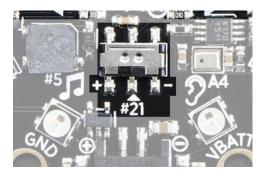

The slide switch is near the center, right above the JST Battery Jack. There's a little nub you can *slide* left or right. This switch is connected to**digital pin #21**. When switched to the left, the value reading is 'high' (thus the + symbol) and when switched right, the value read is 'low' (- symbol).

Library Reference

slideSwitch

You can call CircuitPlayground.slideSwitch() to tell you which way the switch is flipped. It will return **true** if the switch is to the left (+ side) and**false** if the switch is to the right (- side)


leftButton and rightButton

You can ask if the buttons are pressed by callingCircuitPlayground.leftButton() or CircuitPlayground.rightButton(). They will return **true** if and only if the button in question is being

pressed right when the function is called.


NeoPixels

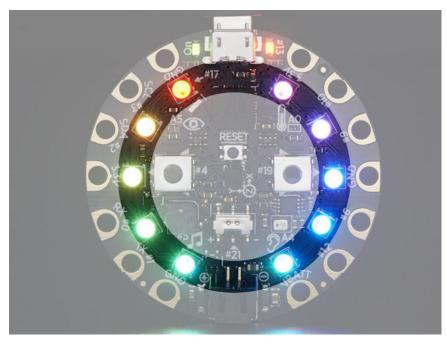One of the fanciest accessories on Circuit Playground are ten (10!) full color LEDs called NeoPixels. Each of these ten Pixels contain bright red+green+blue sub-LEDs and can display any of 16,777,216 different colors!



These pixels are controlled by a single data pin,#17. Unlike non-smart RGB LEDs, you can set the color and a little chip inside the LED will handle the PWM for you.

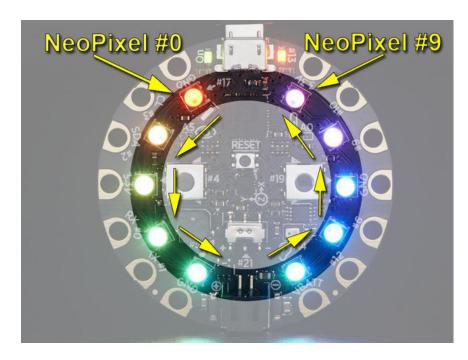Since they are controlled in a *chain*, you will need to tell the Circuit Playground's NeoPixel code which one you want to set the color for. Each NeoPixel is numbered, starting with #0 at the top left and going counter clockwise till you reach #9



Library Reference

setPixelColor

You can set the color for each pixel with the built in NeoPixel library:

CircuitPlayground.setPixelColor(n, red, green, blue)

Where n is between 0 and 9 and indicates which LED you are setting. red/green/blue vary between 0 (off) and 255 (full on)

clearPixels

You can quickly turn all the LEDs off with CircuitPlayground.clearPixels()


setBrightness

By default the *global* brightness of the LEDs is set to 30 out of 255. This means that the LEDs won't be *insanely* bright when you first use them.

You can change the global brightness at the beginning of the sketch (in setup) by running CircuitPlayground.setBrightness(b) where b varies from 0 (no LEDs will ever light) to 255 (incredibly bright!)

setBrightness only affects pixel colors set after it is called. That is, if you set an LED color and then call setBrightness, it wont affect that older LED color. Only going forward will the brightness change to be different.

Temperature Sensor

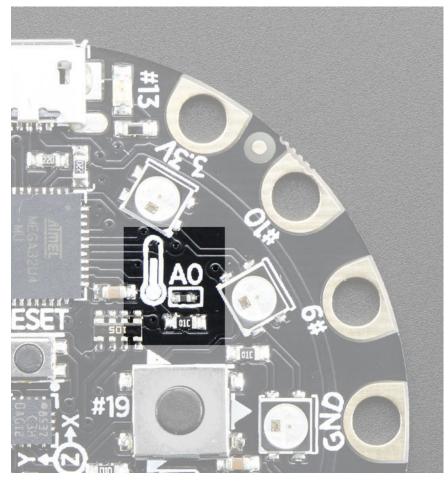

You can sense the temperature using the onboard thermistor. A thermistor is a resistor that changes it's resistance based on the temperature. They are a *little* more complex to use than temperature sensors that spit out Celsius, but they're also much less expensive.


We use the NTC thermistor (Murata NCP15XH103F03RC (http://adafru.it/p3a)) for temperature sensing. While it isn't an all-in-one temperature sensor, with linear output, it's easy to calculate the temperature based on the analog voltage on analog pin #A0. There's a 10K 1% resistor connected to it as a pull down. You can read the analog value and calculate the temperature with the beta-constant (http://adafru.it/p3b), or just use the Circuit Playground library

Library Reference

You can retreive the current calculated temperature with Circuit Playground. temperature() which will return you a floating point number in Centigrade. If you need Fahrenheit use Circuit Playground. temperature F()

© Adafruit Industries ht

Light Sensor

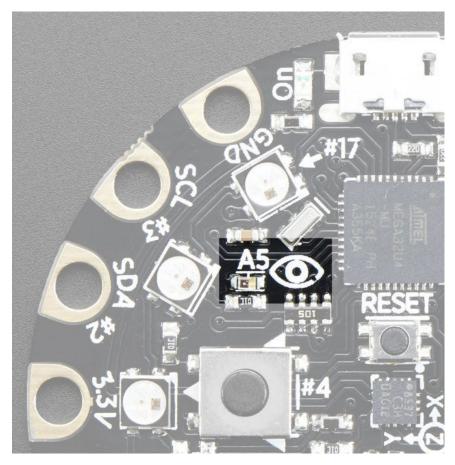

There is an analog light sensor, part number ALS-PT19 (http://adafru.it/n8F), in the top left part of the board. This can be used to detect ambient light, with similar spectral response to the human eye. There is a 10K balancing resistor to convert the current drive to voltage.

This sensor is connect to analog pin #A5, you can use analogRead or the library to read the

analog value. It will read between 0 and 1023 with higher values corresponding to brighter light levels. The range is approximately 0 Lux to 1500 Lux maximum.

1000 Lux will roughly read as 2 Volts (or about 680 as a raw analog reading). A reading of about 300 is common for most indoor light levels. Note that outdoor daylight is 10,000 Lux or even higher, so this sensor is best suited for indoor light levels!

Library Reference

You can request the raw analog reading (0 = no light, up to $1023 = \sim 1500 \text{ Lux}$) with CircuitPlayground.lightSensor()


© Adafruit Industries https://learn.adafruit.com/circuit-playground-lesson-number-0

Page 41 of 83

© Adafruit Industries

https://learn.adafruit.com/circuit-playground-lesson-number-0

Sound Sensor

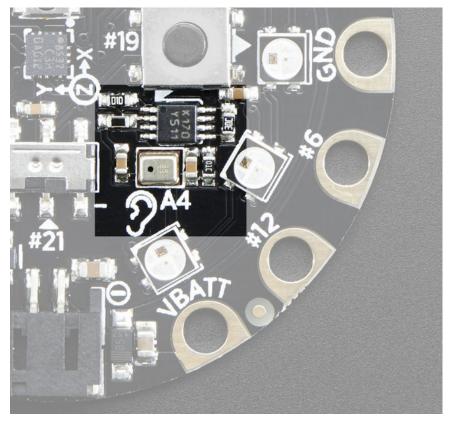

A thin MEMS microphone (http://adafru.it/p3c) can be used to detect audio levels and even perform basic FFT functions. You can read the analog voltage corresponding to the audio on analog pin #A4. Note that this is the raw analog audio waveform! When it's silent there will be a reading of ~330 and when loud the audio will read between 0 and 800 or so. Averaging and smoothing must be done to convert this to sound-pressure-level.


The microphone is sensitive to 100 Hz - 10,000 Hz audio frequencies. See the datasheet

for more details. (http://adafru.it/p3d)

Library Reference

You can read the raw analog value from the amplified microphone with CircuitPlayground.soundSensor() this will give you just a value from between 0 and 1023 where the default 'quiet' voltage is ~330. At this time there is no function for automatic sound pressure level or frequency binning.

Mini Speaker

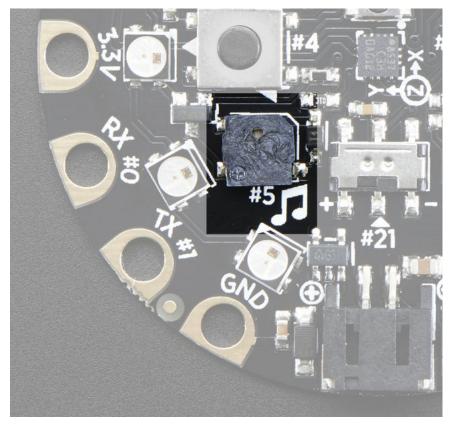

You can make your circuit playground sing with the built in buzzer. This is a miniature magnetic speaker connected to digital pin #5 with a transistor driver. It is quite small but can beep with conviction! It's not good for playing detailed audio, more for beeping and buzzing and simple bleepy tunes.

The driver circuitry is an on/off transistor driver, so you will only be able to play square waves. It is also not the same loudness over all frequencies but is designed to be the


loudest at around 4 KHz. See the datasheet for some more details(http://adafru.it/p3e)

Library Reference

You can play basic square wave beeps/tones with Circuit Playground.play Tone (frequency, duration_ms). Where frequency is the frequency in Hertz and duration is the time to play the beep for, in millisecods.

That means CircuitPlayground.playTone(440, 500) will play 440 Hz (middle A) for 500 milliseconds (half of a second). The call will take the amount of time that it takes to play the tone, so if you have a duration of, say, 5000 milliseconds your Circuit Playground will spend 5 seconds playing a tone and won't be doing anything else.

Accelerometer

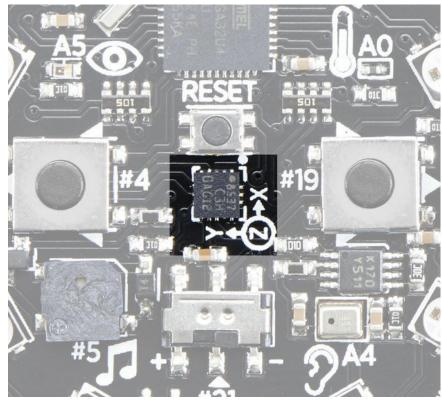

There is a powerful MEMS accelerometer in the very center of your Circuit Playground. This part is the LIS3DH, a 3-axis (X, Y and Z) sensing accelerometer. Accelerometers are the sensors in your WiiMote, phone, and other electronic devices that can sense tilt, gravity, motion and 'tap' effects. These sensors used to cost \$20 each but now are so common we can include them for beginners!

The sensor can sense $\pm 2g$, 4g, 8g (g = 9.8 meters/s²). Of course, at all times on earth you will sense 1 g of gravity!

The LIS3DH is connected to the hardware SPI pins (to leave the I2C pins free) and has the chip select (CS) pin on digital pin #8 and an optional interrupt output on digital pin #7 (also known as IRQ #4)

Library Reference

Motion in X Y and Z

You can ask the sensor for the amount of detected in X, Y and Z directions. Positive values mean acceleration in the direction of the arrow on the silkscreen. For X that means towards the USB jack. For Y that is to the left. For Z that is straight up pointing towards you when looking at the circuit board.

 $\label{localized-control} \mbox{CircuitPlayground.motionX(), CircuitPlayground.motionY(), CircuitPlayground.motionZ()} \ \ \mbox{will each return a floating point value.}$

Setting Accelerometer Range

You can change the range, a smaller range ($\pm 2p$) will give more precision. Larger ranges ($\pm 8g$) can sense greater forces. You can set it whenever you like using CircuitPlayground.setAccelRange(range) where range can be LIS3DH_RANGE_2_G, LIS3DH_RANGE_4_G or LIS3DH_RANGE_8_G

Tap Detection

You can turn on tap detection by calling Circuit Playground.set Accel Tap (taps, threshhold)


Tap detection can detect single taps or 'double taps' (like a double-click). Iftaps is 1 you will only detect single taps, one at a time. If taps is 2, you will be able to detect both single taps and double taps.

You can detect taps in real time by callingCircuitPlayground.getAccelTap(). It will return 0 if no tap is detected, 1 if a single tap is detected, and 2 or 3 if double tap is detected.

The problem with that is you need to query it within about 100 milliseconds of the tapping, which can be difficult to do. If you are comfortable with interrupts you can use the interrupt output to have a function called when a tap is detected: attachInterrupt(digitalPinToInterrupt(7), myfunction, RISING) will call *myfunction* whenever the tap or doubletap occurs.

Alligator Pads & Pinout

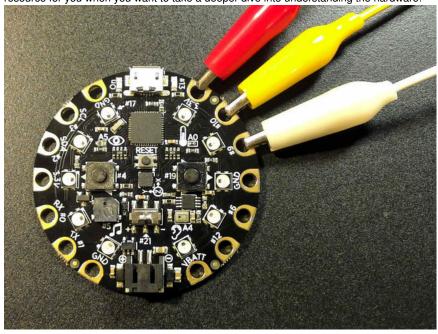Don't feel like you have to understand this part fully! Skim it for now, and consider it a resource for you when you want to take a deeper dive into understanding the hardware!



There are 14 total Alligator Pads on the outside of the Circuit Playground. These are for you when you want to add more sensors or circuitry without the need for soldering. Use any kind of alligator clip (the small ones work best but any size should be able to grip onto the pads)



You can pick up a pack of 12 clips from Adafruit (http://adafru.it/1008)

Capacitive Touch

All 8 non-power pads (e.g. not the GND/3.3V/VBATT) around the Circuit Playground have the ability to act as capacitive touch pads. Each pad has a 1 M Ω resistor between it and digital pin #30. You can toggle this pin in your sketch to control whether the resistor is a pullup or pulldown or floating. Note that this means that all the pads have a 2 M Ω resistance between them, not important for 99% of uses but may be confusing for some cases where you are trying to detect very high resistance values

Library Reference

You can get the capacitance reading from a pin usingCircuitPlayground.readCap(pin) and just set the pin to any of the pad #'s next to the pad (e.g. 0, 1, 2, 3, 6, 9, 10 and 12) The number returned will vary from about 0 to about 1000. Any reading above approximately 50 will correspond to a touch, but it does depend a bit on what material and length is connected to the pin so you will need to adjust your code based on your setup.

Pad Usage (pinout)

We'll use terminology like analog inputs, PWM outputs, interrupts, I2C, UART etc. We'll cover all this later, just know you can use this list for reference!

Left Side

Starting from the Micro USB jack and going clockwise here are what the pins do.

- 3.3V this is the *output* from the onboard 3.3V power supply. This is the main power voltage for the 'Play but can also be used to power sensors, GPS or bluetooth modules, etc. You can draw a maximum of 500mA. See the Battery Jack & Supply page for more details
- #10 this is connected to the microcontroller's pin #10. This pin can also be used for analog inputs and is called A10. It can also act as aPWM output.
- #9 this is connected to the microcontroller's pin #9. This pin can also be used for analog inputs and is called A9. It can also act as a PWM output.
- GND shorthand for Ground you'll need to this when powering or connecting to external devices.
- #6 this is connected to the microcontroller's pin #6. This pin can also be used for analog inputs and is called A7. It can also act as a PWM output.
- #12 this is connected to the microcontroller's pin #12. This pin can also be used for analog inputs and is called A11. It can also act as aPWM output.
- VBATT this is the battery voltage output from whichever is higher: the JST battery pack or USB. It cannot be used as a power input! It is designed to power high-current or high-voltage devices that need more like 5V than 3.3V. If connected to USB, this pin provides 5V. If powered from battery, the output voltage will vary depending on the battery pack.

Right Side

Starting from the Micro USB jack and going counter-clockwise here are what the pins do.


- GND Same as the other Ground pins
- SCL #3 This is a special-purpose pin. It is connected to the microcontroller's pin #3. This pin can also act as a **PWM** output and an **interrupt** input (INT0). The other special usage is connecting to I2C sensors and devices, as the I2C Clock pin
- SDA #2 This is a special-purpose pin. It is connected to the microcontroller's pin #2. This pin can also act as a **PWM** output and an **interrupt** input (INT1). The other special usage is connecting to I2C sensors and devices, as the I2C Data pin
- 3.3V Same as the other 3.3V power supply pins
- RX #0 This is a special-purpose pin. It is connected to the microcontroller's pin #0. This pin can also act as an **interrupt** input (INT2). The other special usage is connecting to UART/Serial sensors and devices, as the Data Receive (RX) pin.
- TX #1 This is a special-purpose pin. It is connected to the microcontroller's pin #1. This pin can also act as an **interrupt** input (INT3). The other special usage is connecting to UART/Serial sensors and devices, as the Data Transmit (TX) pin.
- GND Same as the other Ground pins

Page 51 of 83

Power Up Test

Now we are ready for the moment of truth, it's time to plug your Circuit Playground in and power it up. The easiest way to do this is to plug one end of the USB cable into the 'Play and the other end into a computer. The computer will then power the Circuit Playground.

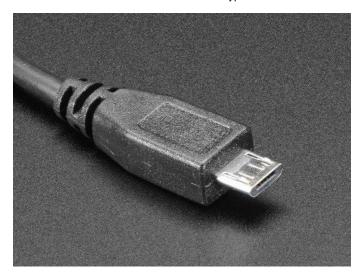
You'll need a USB cable with a slim Micro B-type end:



Make sure that the USB cable is plugged in directly to a computer port. Sometimes monitors or keyboards have a USB port you can plug into. Most of the time this is fine, but I strongly suggest you plug it directly into the computer as that will eliminate any possible problems. Same goes for USB hubs - skip those for now and go direct


Later on, once you've verified you can power the Circuit Playground and upload sketches no problem, then you can try plugging it into other ports.

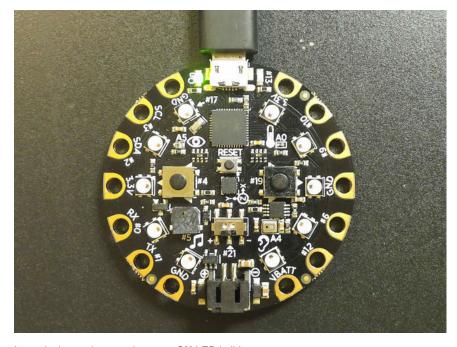OK anyways, so plug int he USB cable and check that your board looks like this:



In particular, make sure the green ON LED is lit!

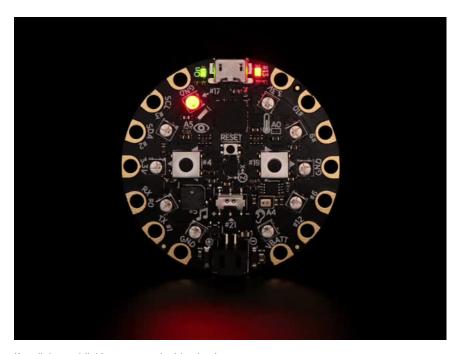If this is the first time you're plugging in your Circuit Playground fresh from the factory, the red **L** LED and and NeoPixels might also be lit or blinking - this is normal.



If no lights or blinking occurs, double check:


- Is the USB cable plugged into the computer and into the Circuit Playground?
- Try another USB cable
- Check there's nothing metallic touching the Circuit Playground that could beshorting out the device
- Is the computer on?
- Try another USB port, USB cable, and computer?

If you still can't get it working, your Circuit Playground may be faulty and need replacement!

Bootloader Reset Test

Next up, you can do a quick **bootloader test** - this will let you know that the Circuit Playground chip has been programmed with a bootloader which is required!

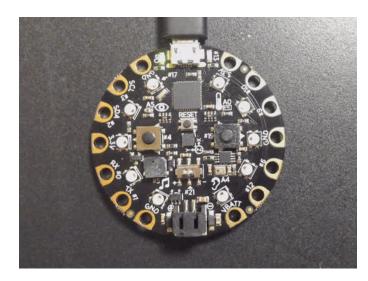While powered, <u>double click</u> the **Reset button** - you will see the**#13** red LED breathe/pulse on and off. It will pulse about 10 times, once per second



If you get both the green **ON** LED lit and the red#13 LED to pulse you are well on your way and have passed the power up test!